


# EE5311 Tutorial\_6b Report

L.Pradeep EE22B074


2. Draw the schematic of a 8-bit ripple-carry adder using the above mirror-symmetric full adder and trace its critical path.
  - (a) Measure the delay of the critical path if the MSB sum and carry bits ( $S_7, C_7$ ) drive a unit inverter each.
  - (b) Compare the measured delay with the delay estimated using logical/electrical/branching effort.
  - (c) Draw the layout of the complete ripple-carry adder using the above full-adder layout and inverter layout from Assignment 5. Ensure that aspect ratio (width/height) of your layout is in the range [0.9, 1.1]. Measure the layout extracted delay and compare it with the pre-layout delay.
 
## Critical Path

- The **critical path** is the longest delay path.
- In RCA, it's from **Cin** → **C1** → **C2** → ... → **C7** → **S7**.
- The delay adds up due to carry propagation through all 8 stages.



```
Reference value : 9.67960e-09
No. of Data Rows : 1040
Warning: No job (tran, ac, op etc.) defined:
run simulation not started
tpdh          = 2.143338e-09 targ= 2.148338e-09 trig= 5.000000e-12
tpdhl         = -1.889691e-09 targ= 1.253093e-10 trig= 2.015000e-09
tpd_sumh      = 3.185212e-10 targ= 3.235212e-10 trig= 5.000000e-12
tpd_suml      = 3.386688e-10 targ= 2.353669e-09 trig= 2.015000e-09
Delay from Cin to C7: 1.26825E-10
Delay from Cin to S7: 3.28595E-10
ngspice 7 -> █
```

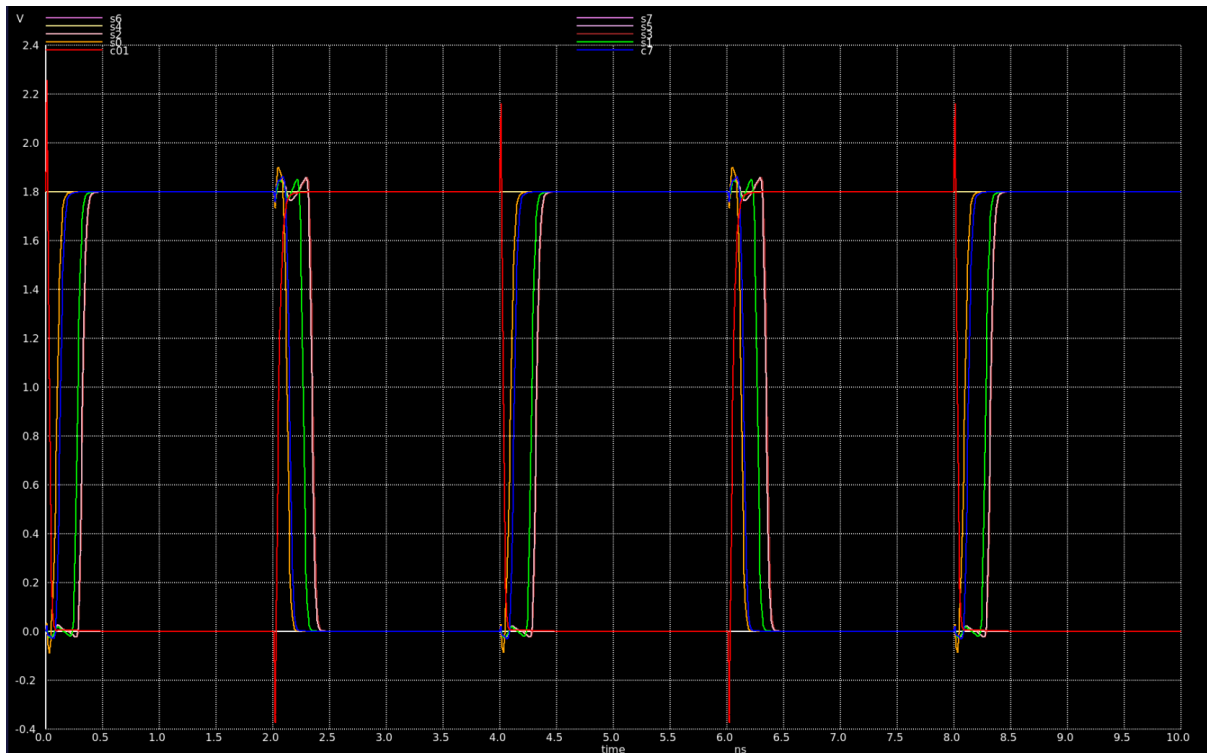

## (b) Compare Delay with Logical/Electrical/Branching Effort

- Logical Effort (LE):** An estimation technique using logical effort ( $g$ ), parasitic delay ( $p$ ), and electrical effort ( $h = C_{load} / C_{in}$ ).
- For RCA:
  - Each full adder stage has  $g \approx 1$  for carry path.
  - Let  $p \approx 1$  and fanout  $\approx 1$  (as load is a unit inverter).
- Total delay:  
 $D = N \times (g \cdot h + p)$   
 For  $N = 8$ :  
 $D_{LE} = 8 \times (1 \cdot 1 + 1) = 16 \text{ units}$

