 



EE5311 Tutorial2


L.Pradeep EE22B074

1. Size the pMOS transistor so that $V_{OL} = 0.1V$. Using Ngspice, plot the DC transfer characteristic.



derivative and low noise margins

 

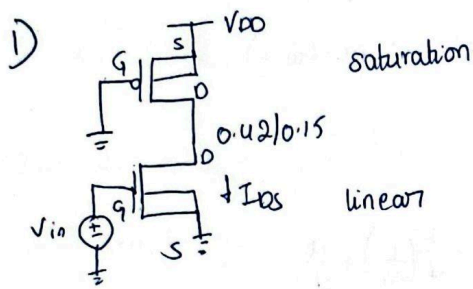

$$(I_{D,min})_n = (I_{D,sat})_p$$

$$\left(\frac{W_p}{L_p}\right) \mu_n C_{ox} n \left(\frac{V_{GS} - V_{TH}}{1 + \frac{V_{DS}}{E_{CL}}} \right) V_{DS} (1 + \lambda V_{DS}) = \frac{\mu_p C_{ox} p}{2} (V_{GS} - V_{TP})^2 (1 + \lambda V_{DS}) \times \frac{E_{CL}}{E_{CL} + V_{GS} - V_{TP}} \left(\frac{W_p}{L_p}\right)$$

$$25 \times 834 \times 2.8 \left(\frac{1.1}{1.1} \right) \times 0.1 \times (1.018) = \frac{9 \times 816}{2} (1.1)^2 (1 + 0.306) \times \frac{0.83}{1.93} \left(\frac{W_p}{0.15} \right)$$

$$W_p = \frac{50 \times 834 \times 2.8 \times 0.11 \times 1.018 \times 1.93 \times 0.15}{9 \times 816 \times 1.306 \times 0.83 \times 1.1 \times 1.21} = \frac{3785}{7960 \times 1.21} = \frac{0.42}{1.21} \mu m$$

for $L = 0.3 \mu m$

$$W_p = \frac{0.34 \times 0.42 \times 2}{0.62} = 0.46$$

$$(W/L)_p = 1.53$$

Using SPARSE 1.3 as Direct Linear Solver

Reference value : 0.00000e+00

No. of Data Rows : 181

vil = 7.712411e-01

vih = 1.191576e+00

vm = 1.058823e+00

NML: 0.771241 NMH: 0.608424

ngspice 7 -> █

(a) Find the inverter threshold voltage. (b) Plot the derivative and obtain the high and low noise margins. Do an approximate calculation using the analytical models and compare with the simulated value. (c) Assuming $V_{in} = V_{DD}$, find the average power dissipated and compare with the analytically obtained value

$$a) V_{inv} = \frac{\sqrt{K_r}}{\sqrt{K_r} + 1} (V_{DD} - V_{TP}) + \frac{V_{TP}}{1 + \sqrt{K_r}}$$

$$K_r = \frac{K_p(W/L)_p}{K_n(W/L)_n} = \frac{1.53 \times 9 \times 816}{2.8 \times 25 \times 834} = \frac{11236}{58380} = 0.19$$

$$V_{inv} = \frac{0.43}{1.43} (1.1) + \frac{0.7}{1.43} = \frac{1.18}{1.43} = 0.82V$$

$$b) V_{IH} = V_{th} + \frac{2V_{out}}{2R_L K_n(W/L)_n}$$

$$= 0.7 + 0.2 - \frac{1}{2 \times 26 \times 10^3 \times 0.025 \times 0.0082 \times 2.8}$$

$$= 0.7 + 0.2 - \frac{1}{15.17} = 0.9 - 0.06 = 0.84V$$

$$V_{IL} = V_{th} + \frac{1}{R_L(2K_n(W/L)_n)} = 0.7 + 0.06 = 0.76V$$

$$c) P_{dis} = V_{in} I_{ds} = V_{in} \left[\left(\frac{W}{L} \right)_p \times \frac{\mu_p C_{ox}}{2} (V_{GS} - V_{TP})^2 (1 + \lambda V_{DS}) \times \frac{E_{PL}}{E_L + V_{GS} - V_{TP}} \right]$$

$$= 1.8 \times \left[1.53 \times \frac{9 \times 816}{2} \times 0.62 \times 1.306 \times 1.21 \right] \times 10^{-8}$$

$$= 1.8 \times [55 \mu A]$$

$$= 100 \mu W$$

$$= 0.1 mW$$


Power according to the simulated is IV

$I = 45 \mu A$


$V = 1.8V$

Power = 0.8mW

 2. inverter threshold voltage $V_{inv} = V_{DD}/2$. And DC transfer characteristic.




derivative and obtain the noise margins

 

```
Using SPARSE 1.3 as Direct Linear Solver
Reference value : 0.00000e+00
No. of Data Rows : 181
vil          = 7.712492e-01
vih          = 1.030598e+00
vm           = 9.030870e-01
NML: 0.771249 NMH: 0.769402
ngspice 7 -> █
```

2

 

a) $V_{inv} = V_{DD}/2$

$$V_{inv} = \frac{\sqrt{K_r}}{\sqrt{K_r} + 1} (V_{DD} - V_{TH}) + \frac{V_{TH}}{\sqrt{K_r} + 1}$$

$$0.9 = \frac{1.1\sqrt{K_r} + 0.7}{1 + \sqrt{K_r}} \Rightarrow \frac{0.9}{1.1 + 0.9\sqrt{K_r}} = 1.1\sqrt{K_r} + 0.7$$

$$0.2\sqrt{K_r} = 0.2 \Rightarrow K_r = \frac{1.21}{0.49} = 2.46 \quad K_r = 1$$


$$K_r = \frac{K_p(W/L)_p}{K_n(W/L)_n} \Rightarrow$$

$$\Rightarrow (W/L)_p = \frac{K_n}{K_p} (W/L)_n = \frac{25 \times 834}{9 \times 816} (W/L)_n$$


$$(W/L)_p = 2.83 \left(\frac{W}{L}\right)_n = 7.9$$

CS Scanned with CamScanner


(W/L)_p is increased by a factor of 10

 

$(W/L)_p$ is constant

 


Decreased by a factor of 10

 

- **Increasing $(W/L)_p$ by a factor of 10:**
 - The PMOS transistor becomes stronger (higher drive current for the same V_{gs}).
 - The transition region shifts towards lower V_{in} , meaning V_{inv} decreases.
 - The slope of the DC transfer characteristic becomes steeper, which may improve noise margins.
- **Decreasing $(W/L)_p$ by a factor of 10:**
 - The PMOS transistor becomes weaker.
 - The transition region shifts towards higher V_{in} , meaning V_{inv} increases.
 - The slope of the DC transfer characteristic becomes shallower, reducing noise margins.

In summary, increasing $(W/L)_p$ shifts the threshold voltage downward, while decreasing it shifts the threshold upward.

 DC transfer characteristic for VDD ranging from 0.2V to 1.8V in steps of 0.2V.




Evaluating for Different V_{DD} Values:

- At very low V_{DD} (e.g., 0.2V), both NMOS and PMOS may operate in subthreshold regions, leading to a poor transition.
- At higher V_{DD} (e.g., 1.8V), the transistors operate in strong inversion, leading to a well-defined switching behavior.

Adjusting $(W/L)_p$ to Achieve $V_{inv} \approx V_{DD}/2$:

- If V_{inv} is too high, increase $(W/L)_p$ to strengthen PMOS.
- If V_{inv} is too low, decrease $(W/L)_p$ to weaken PMOS.

 I_{ds} vs V_{in} for $V_{DD} = 0.2, 0.8, 1.8V$.



Peak I_{ds} Values

Using SPARSE 1.3 as Direct Linear Solver

No. of Data Rows : 221

imax: 1.19233E-12 2.98999E-11 4.32958E-10