
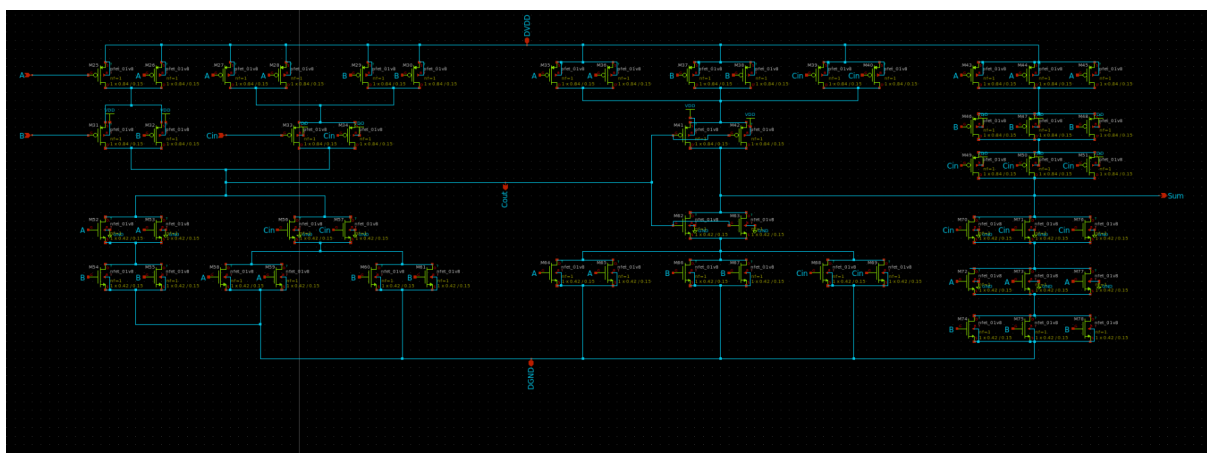
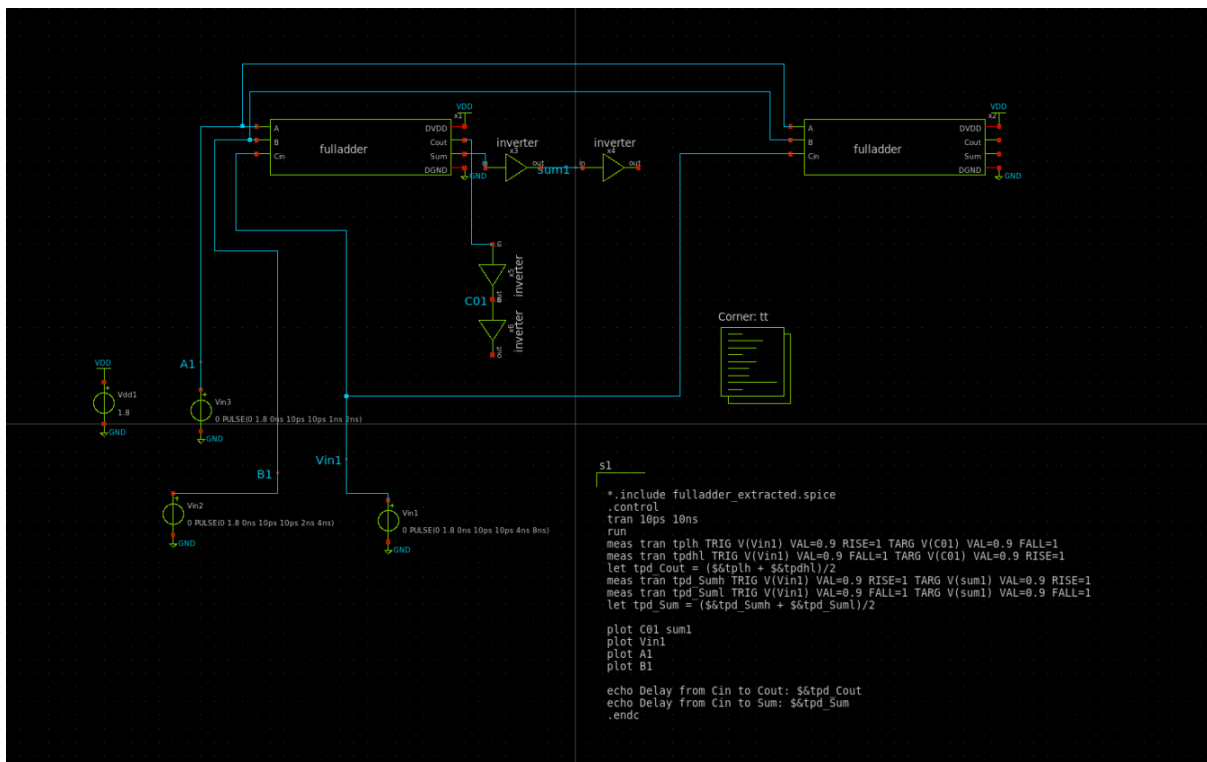


# EE5311 Tutorial\_6a

## L.Pradeep EE22B074

 1. Draw schematic for the carry and sum logic in a mirror-symmetric full adder done in class. Size the p/nMOS to minimize the delay from input to output carry and the stage effort of the carry logic is four when used in a ripple carry adder. Create a symbol for the full adder and connect two full adders as shown below:




(a) Measure the delays: (i) from  $C_{-1}$  to  $\overline{C_0}$ , and (ii) from  $C_{-1}$  to  $\overline{S_0}$ .


```

Reference value : 8.23960e-09
No. of Data Rows : 1040
Warning: No job (tran, ac, op etc.) defined:
run simulation not started
tplh          = 2.727253e-11 targ= 3.227253e-11 trig= 5.000000e-12
tpdhl         = 3.335492e-11 targ= 2.048355e-09 trig= 2.015000e-09
tpd_sumh      = 2.076368e-09 targ= 2.081368e-09 trig= 5.000000e-12
tpd_suml      = -1.976783e-09 targ= 3.821670e-11 trig= 2.015000e-09
Delay from Cin to Cout: 3.03137E-11
Delay from Cin to Sum: 4.9795E-11
ngspice 7 -> █

```

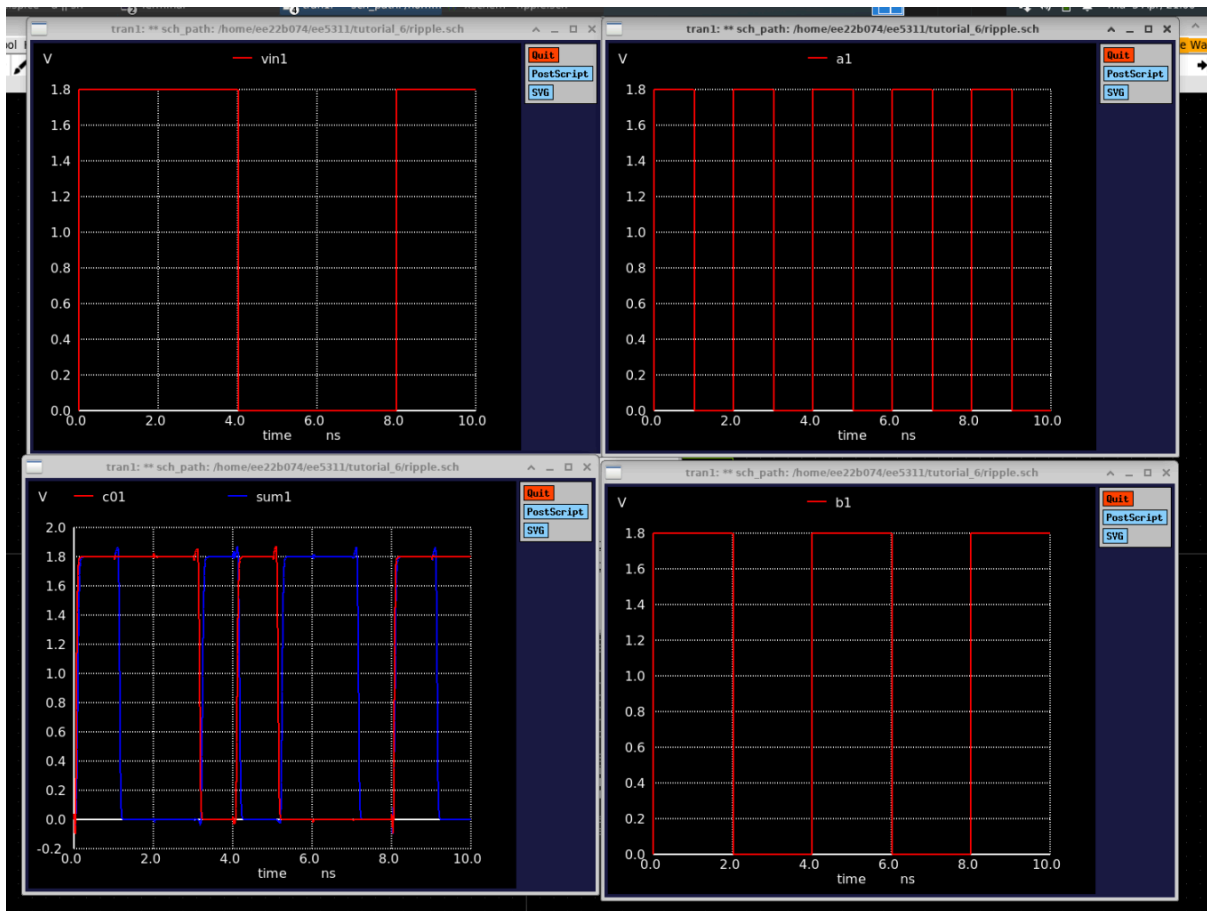

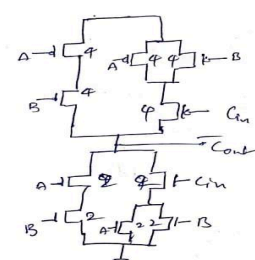(b) How do the measured delays compare against that estimated using logical and electrical effort?



Calculating the delay from  $C_{in}$  to  $C_{out}$

input Capacitance =  $6C$

logical effort =  $\frac{6C}{3C} = 2$

$g = 2$

Electrical effort  $h = 1$

Parasitic effort =  $3 \frac{12C}{3C}$

$P = 4$

Parasitic effort =  $\frac{\text{output Cap}}{3C} = \frac{12C}{3C} = 4$

$g = 2, P = 4, h = 1$

$d = gh + P$

$d = 2 + 4$

$d = 6$

total delay =  $6 \times (\text{delay of unit inverter of same drive strength})$

$= 6 \times 2 \times 10^{-11}$

delay =  $12 \times 10^{-11} \text{ s}$

from  $C_{in}$  to  $C_{out}$

delay calculation (Cin to Sum)

Calculation of logical effort

$$g = \frac{6 + 4}{3} = \frac{10}{3}$$

$$h = \frac{(3 + 2) \cdot 2}{10} = 1 \frac{10}{10} = 1$$

$$P = \frac{10}{3} = 1 \frac{10}{3}$$

$$\text{delay} = gh + P$$

$$= \frac{10}{3} + 1 \frac{10}{3} = \frac{20}{3}$$

$$d = \frac{20}{3} \times 2 \times 10^{-11}$$

$$d = \frac{40}{3} \times 10^{-11} = 13.33 \times 10^{-11}$$

$$d = 1.33 \times 10^{-10} \text{ Sec}$$


delay from  $C_{in}$

total delay from Cin to Sum

$$\text{delay} = 1.33 \times 10^{-10} + 1.2 \times 10^{-10}$$

$$\text{delay} = 2.53 \times 10^{-10} \text{ sec}$$

 
- (c) Draw the layout for the full-adder and measure the layout extracted delay and compare it against the pre-layout delay. Use diffusion sharing and num fingers to create a compact layout. The height of the full adder should be the same as the inverter in Assignment 5.



```

Reference value : 9.97200e-09
No. of Data Rows : 1037
Warning: No job (tran, ac, op etc.) defined:
run simulation not started
tphl      = 3.753856e-11 targ= 4.253856e-11 trig= 5.000000e-12
tpdhl     = 5.204765e-11 targ= 2.067048e-09 trig= 2.015000e-09
tpd_sumh  = 2.103724e-09 targ= 2.108724e-09 trig= 5.000000e-12
tpd_suml  = -1.922801e-09 targ= 9.219862e-11 trig= 2.015000e-09
Delay from Cin to Cout: 4.47931E-11
Delay from Cin to Sum: 9.046E-11
ngspice 7 -> █

```

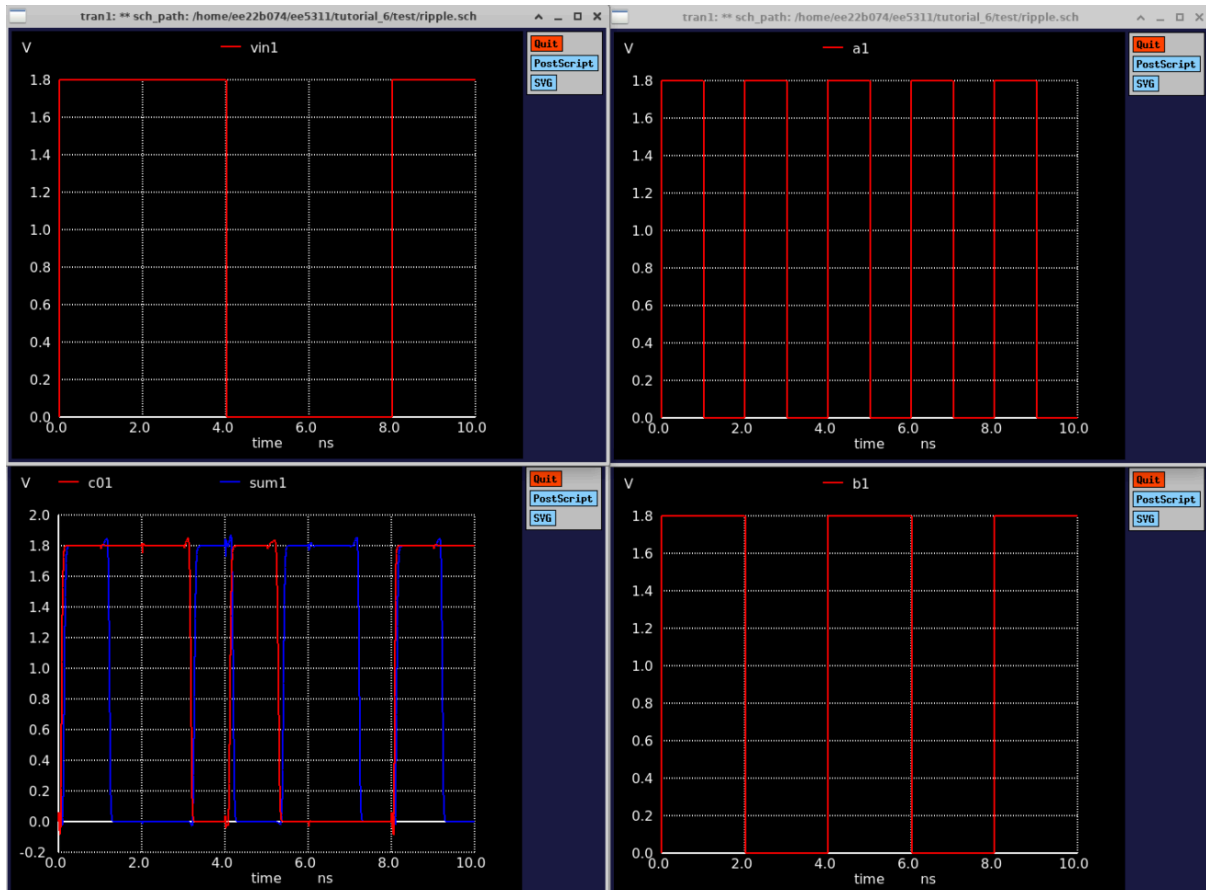

## Stick Diagrams

