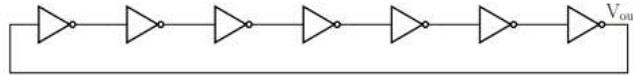


# EE5311 Tutorial\_4 Report

L.Pradeep EE22B074


1. Using the CMOS inverter with the minimum delay from Assignment 3, construct a seven stage ring oscillator as shown below and find the oscillating frequency.



To ensure oscillation in the transient simulation, set the node  $V_{out} = 0V$  initially using: `.ic v(Vout)=0`

- (a) Measure the oscillating frequency for  $V_{DD} = 1.8V$ .


## Part -B : SCHEMATIC

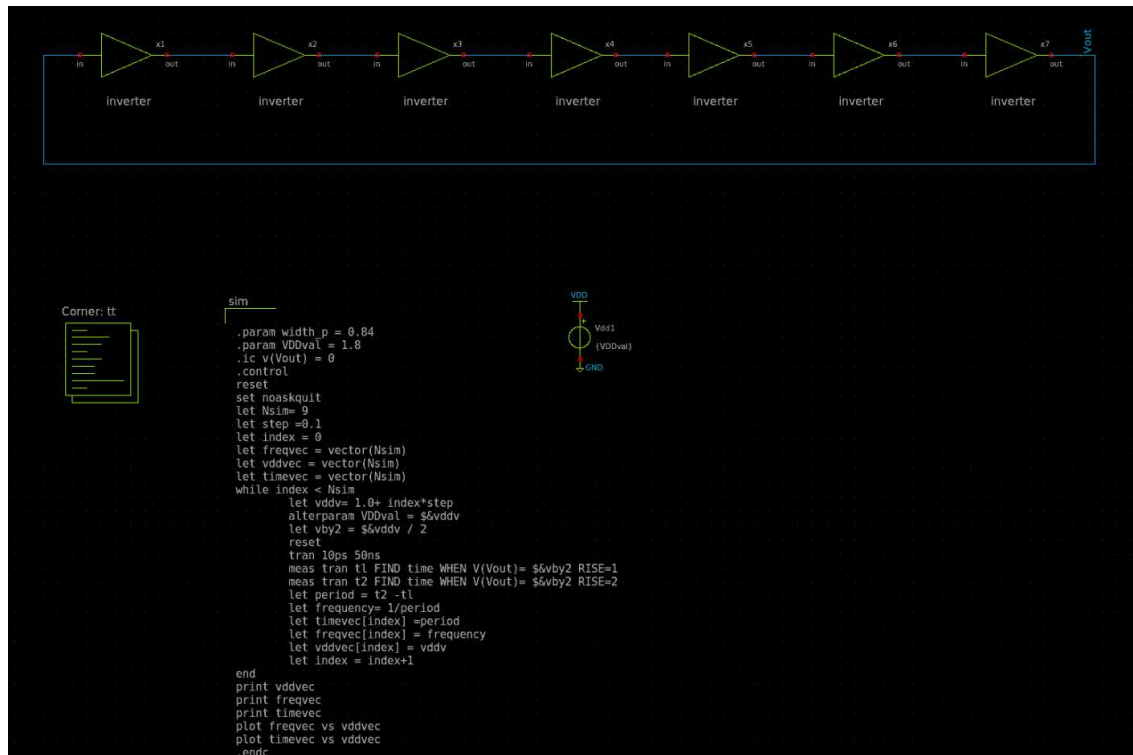

period = 4.124471e-10  
frequency = 2.424553e+09

(b) Plot the oscillating frequency and time period as a function of  $V_{DD}$  for  $V_{DD} = 1V$  to  $1.8V$  in steps of  $0.1V$ .

Measurements: B) Graph Time vs VDD

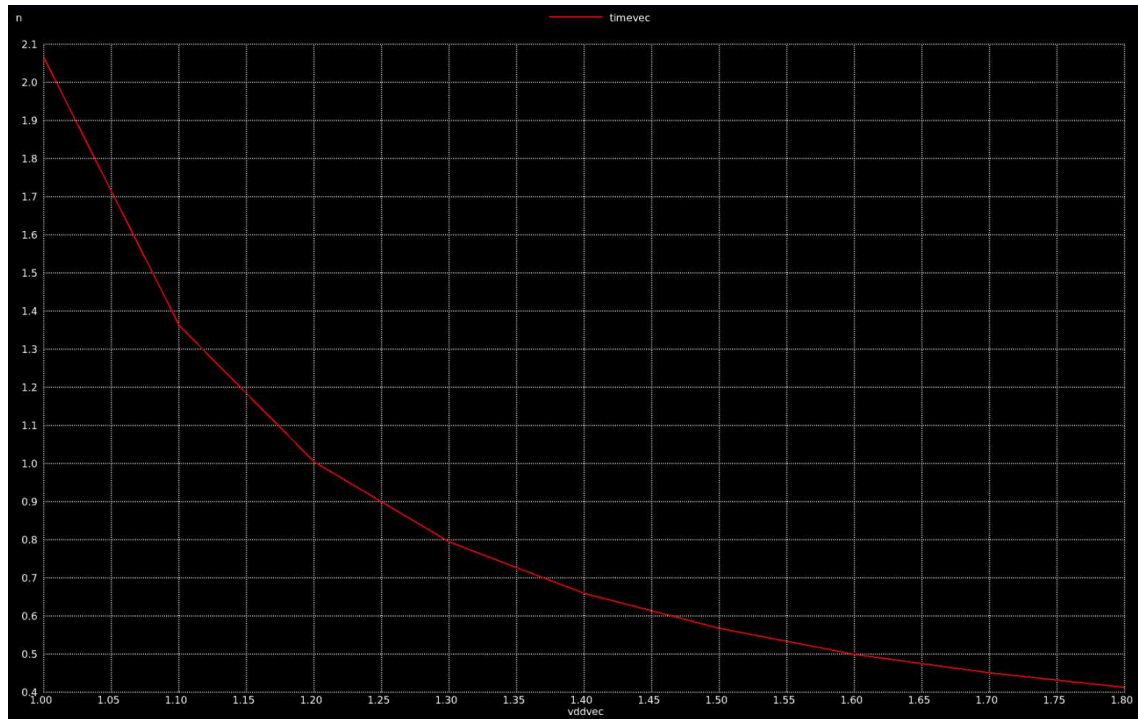


Frequency vs vDD




(c) Repeat the experiment (b) with nine inverter stages.

## PART -C : SCHEMATIC

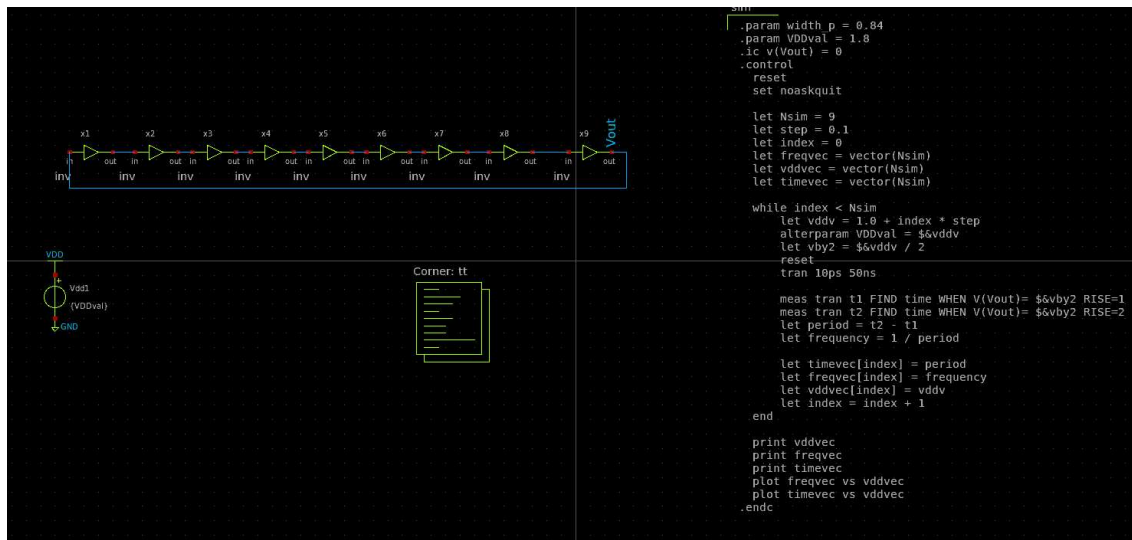

## C) Frequency vs VDD

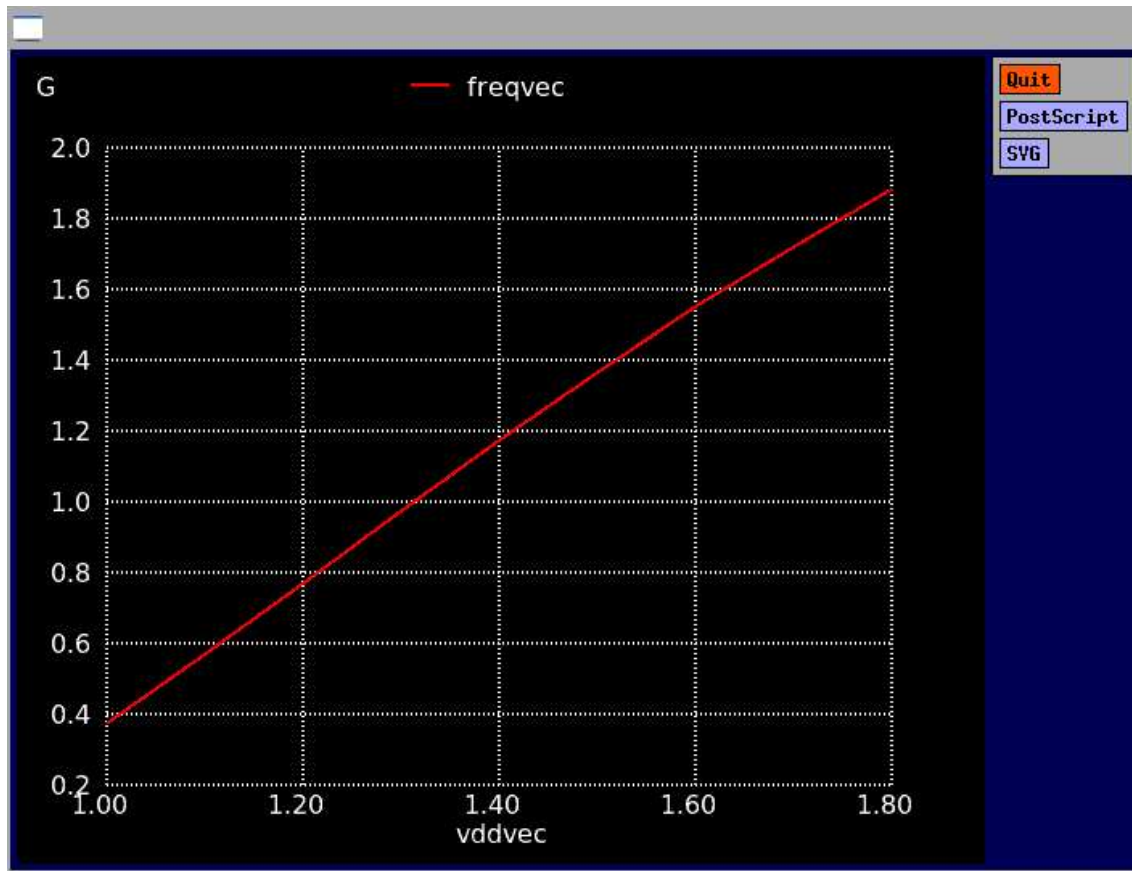

### C) Time vs VDD

