 


EE5311 Tutorial_5 Report

L.Pradeep EE22B074


1. Draw a DRC and LVS clean layout of the CMOS inverter with the minimum delay from Assignment 3.


(a) Extract the parasitic values from the layout and find the delay of the inverter using the circuit:



(b) Measure the delay including the layout parasitic of net V_{out} .

Layout of CMOS inverter

 

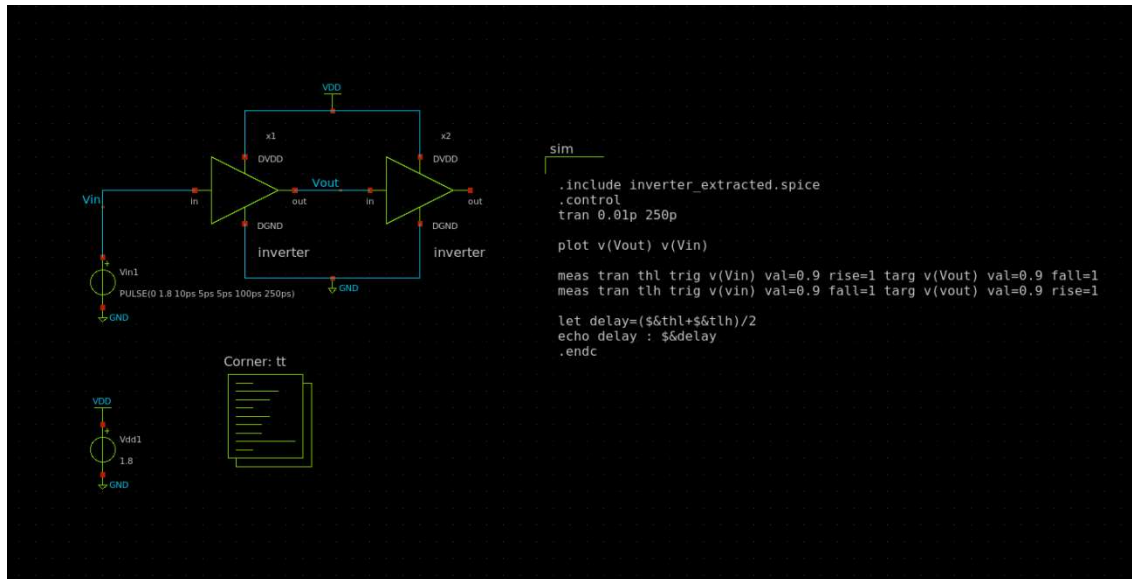

Delay before the parasitic capacitances = $2.07\text{e-}11$

Initial Transient Solution

Node	Voltage
vout	1.8
vin	0
vdd	1.8
net1	$3.1174\text{e-}07$
vdd1#branch	$-3.21945\text{e-}10$
vin1#branch	0

Reference value : $2.36045\text{e-}10$

No. of Data Rows : 25020

thl = $1.189162\text{e-}11$ targ= $2.439162\text{e-}11$ trig= $1.250000\text{e-}11$

tlh = $2.962604\text{e-}11$ targ= $1.471260\text{e-}10$ trig= $1.175000\text{e-}10$

delay : $2.07588\text{E-}11$

ngspice 7 -> █

Parasitic values of the given cmos from the extracted file

R0 in.n0 in.t0 249.532

R1 in.n0 in.t1 193.299

R2 in in.n0 158.875

R3 DVDD DVDD.t0 949.322

R4 DVDD DVDD.t1 398.459

R5 out out.t1 408.697

R6 out out.t0 280.94

R7 DGND DGND.t0 4634

R8 DGND DGND.t1 278.224

C0 out DVDD 0.102731f

C1 in DVDD 0.106389f

C2 out in 0.039402f

C3 out DGND 0.124072f

C4 in DGND 0.227955f


C5 DVDD DGND 0.773996f

Delay after the parasitic capacitances = $2.49\text{e-}11$

```
Circuit: ** sch_path: /home/ee22b074/ee5311/tutorial_5/tb.sch
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
Using SPARSE 1.3 as Direct Linear Solver
Initial Transient Solution
-----
Node                                Voltage
-----
x1.out,t1                           1.8
x1.in,t0                             0
x1.dvdd,t1                           1.8
x1.dvdd,t0                           1.8
x1.out,t0                            1.8
x1.in,t1                              0
x1.dgnd,t1                           9.78908e-12
x1.dgnd,t0                           8.34439e-09
x1.in,n0                              0
vin                                  0
vdd                                  1.8
vout                                  1.8
x2.out,t1                           7.9196e-07
x2.in,t0                              1.8
x2.dvdd,t1                           1.8
x2.dvdd,t0                           1.8
x2.out,t0                           6.25287e-07
x2.in,t1                              1.8
x2.dgnd,t1                           6.72417e-08
x2.dgnd,t0                           3.27277e-15
x2.in,n0                              1.8
net1                                6.93185e-07
vdd1#branch                         -2.43518e-10
vin1#branch                           0

Reference value : 2.19235e-10
No. of Data Rows : 25020
thl      = 2.254870e-11 targ= 3.504870e-11 trig= 1.250000e-11
tlh      = 2.742707e-11 targ= 1.449271e-10 trig= 1.175000e-10
delay : 2.49879E-11
ngspice 7 -> █
```

 2. Using the inverter layout above, draw the layout of a seven stage ring oscillator shown below.





To ensure oscillation in the transient simulation, set the node $V_{out} = 0\text{V}$ initially using: `.ic v(Vout)=0`


- Measure the oscillating frequency for $V_{DD} = 1.8\text{V}$ with the layout parasitics.
- Plot the oscillating frequency and time period as a function of V_{DD} for $V_{DD} = 1\text{V}$ to 1.8V in steps of 0.1V .
- Compare the frequencies against pre-layout simulation in Assignment 4.

oscillating frequency for $V_{dd}=1.8$ with the layout parasitics


Frequency = $3.59\text{e}+08$

 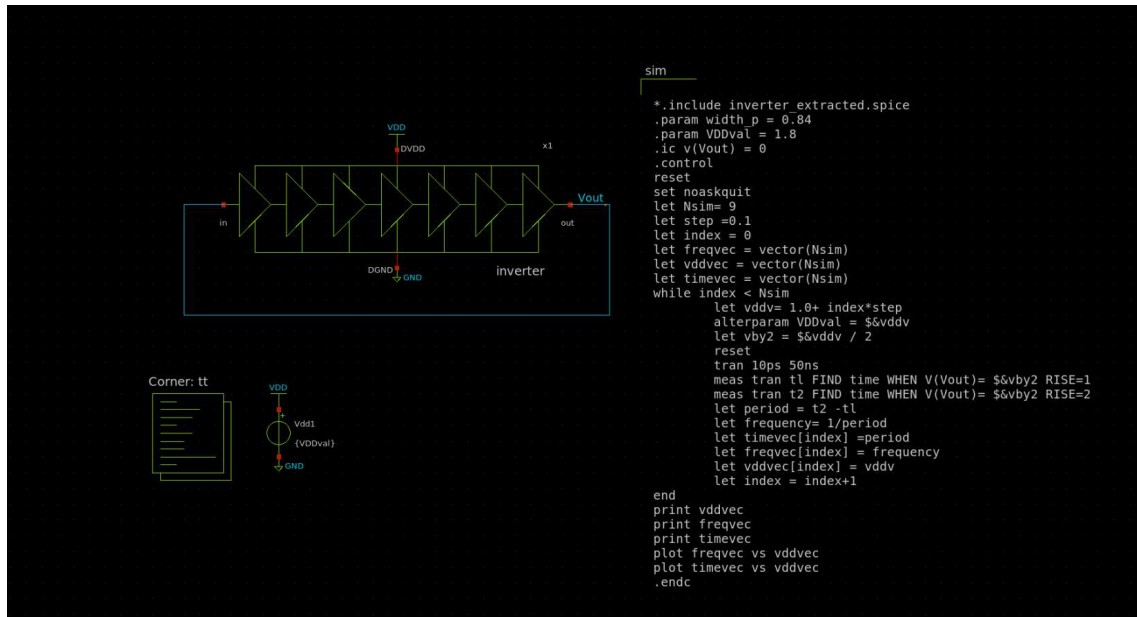

frequency vs Vdd

 

Time period vs Vdd

 


Values of frequency and time period with parasitic values

		Constant values
		constants Wed Jan 22 06:48:28 UTC 2025
Index	vddvec	
0	1.000000e+00	
1	1.100000e+00	
2	1.200000e+00	
3	1.300000e+00	
4	1.400000e+00	
5	1.500000e+00	
6	1.600000e+00	
7	1.700000e+00	
8	1.800000e+00	
		Constant values
		constants Wed Jan 22 06:48:28 UTC 2025
Index	frequenc	
0	3.597717e+08	
1	5.496954e+08	
2	7.516428e+08	
3	9.568004e+08	
4	1.159311e+09	
5	1.356036e+09	
6	1.544175e+09	
7	1.722834e+09	
8	1.890524e+09	
		Constant values
		constants Wed Jan 22 06:48:28 UTC 2025
Index	timevec	
0	2.779541e-09	
1	1.819189e-09	
2	1.330419e-09	
3	1.045150e-09	
4	8.625811e-10	
5	7.374355e-10	
6	6.479952e-10	
7	5.804389e-10	
8	5.289539e-10	

Values of frequency and time period with out parasitic values

Index	vddvec
0	1.000000e+00
1	1.100000e+00
2	1.200000e+00
3	1.300000e+00
4	1.400000e+00
5	1.500000e+00
6	1.600000e+00
7	1.700000e+00
8	1.800000e+00
Constant values constants Med Jan 22 06:48:28 UTC 2025	
Index	frequvec
0	4.410665e+08
1	6.774513e+08
2	9.318293e+08
3	1.192913e+09
4	1.453660e+09
5	1.710315e+09
6	1.955931e+09
7	2.188518e+09
8	2.414532e+09
Constant values constants Med Jan 22 06:48:28 UTC 2025	
Index	timevec
0	2.267232e-09
1	1.476121e-09
2	1.073158e-09
3	8.382838e-10
4	6.879189e-10
5	5.846876e-10
6	5.112497e-10
7	4.569302e-10
8	4.141589e-10

ngspice 7 -> █

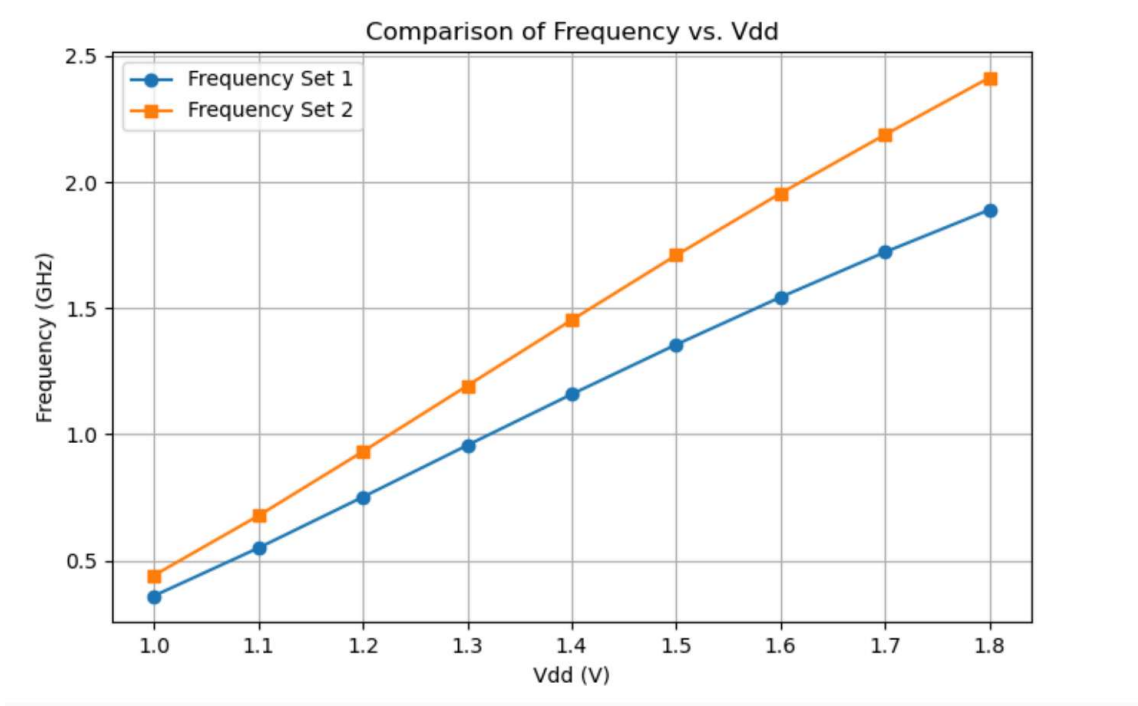

Frequency set 1 : frequency of the ring oscillator without the layout capacitance
Frequency set 2 : frequency of the ring oscillator with the layout capacitance